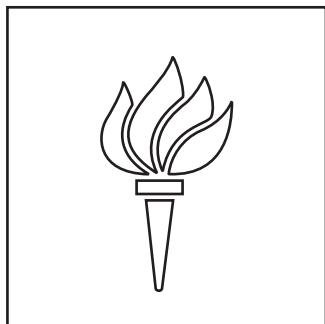





ARP 2600



NYU


Ability
Project



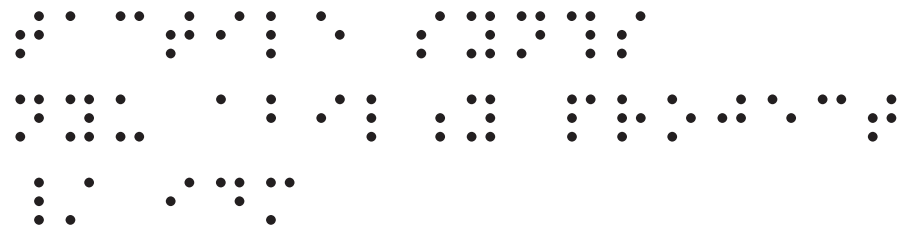

Tactile Synths

NYU Ability Project / IDM

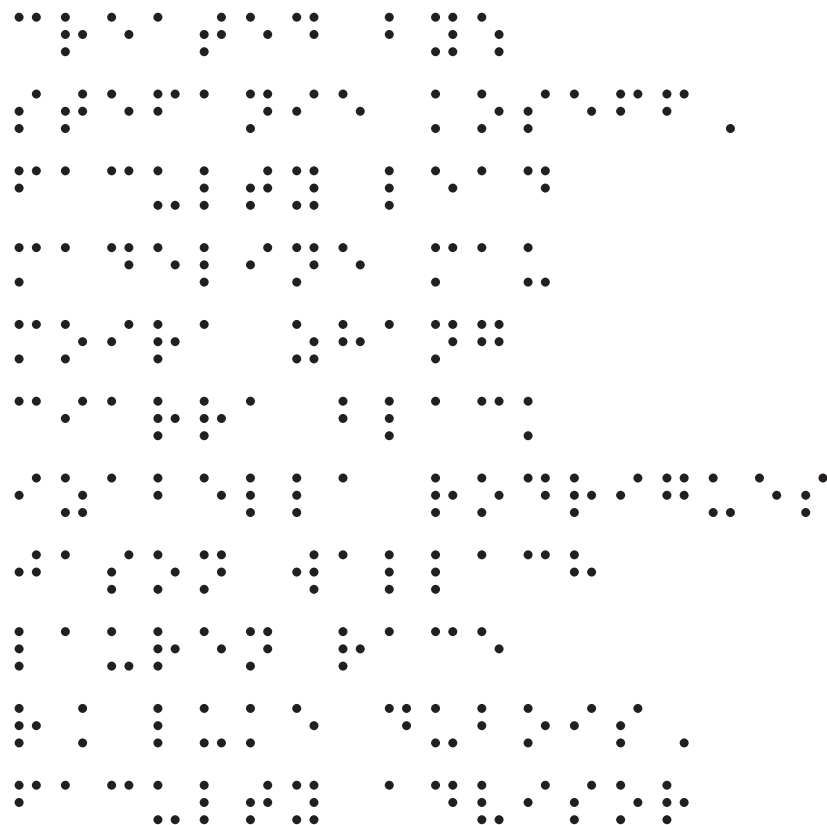

Created by:

Stefanie Koseff, Faculty Lead

Madeline Mau

Moirra Zhang

Ciarra Black

Izabella Rodrigues

Jason Wallach

Lauren Race

R. Luke Dubois, Faculty Advisor



1. The first row of the tactile synth contains 16 groups of dots, each group representing a character. The groups are arranged in a single line. The second row contains 16 groups of dots, each group representing a character. The third row contains 16 groups of dots, each group representing a character. The fourth row contains 16 groups of dots, each group representing a character. The fifth row contains 16 groups of dots, each group representing a character. The sixth row contains 16 groups of dots, each group representing a character.

2. The first row of the tactile synth contains 16 groups of dots, each group representing a character. The second row contains 16 groups of dots, each group representing a character. The third row contains 16 groups of dots, each group representing a character. The fourth row contains 16 groups of dots, each group representing a character. The fifth row contains 16 groups of dots, each group representing a character. The sixth row contains 16 groups of dots, each group representing a character.

Tactile Synths © 2025 New York University is licenced under CC BY-NC-SA 4.0.

To view a copy of this licence, visit

<https://creativecommons.org/licenses/by-nc-sa/4.0/>

Part of the Synth Access Project.

GitHub: <https://github.com/IDMNYU/synthaccess>



Knob



Button



ST - Sawtooth



TRI - Triangle



Sine



SQ - Square




PLS - Pulse



ADSR

VCO-1

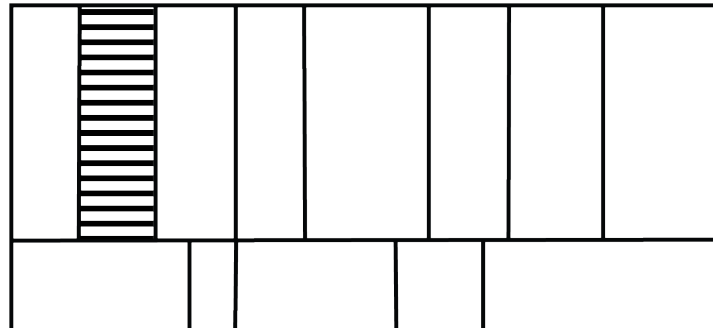

Frequency

Fine Tune

ST



VCO-1

PLS


● ● ●

● ● ●

● ● ●



LFO

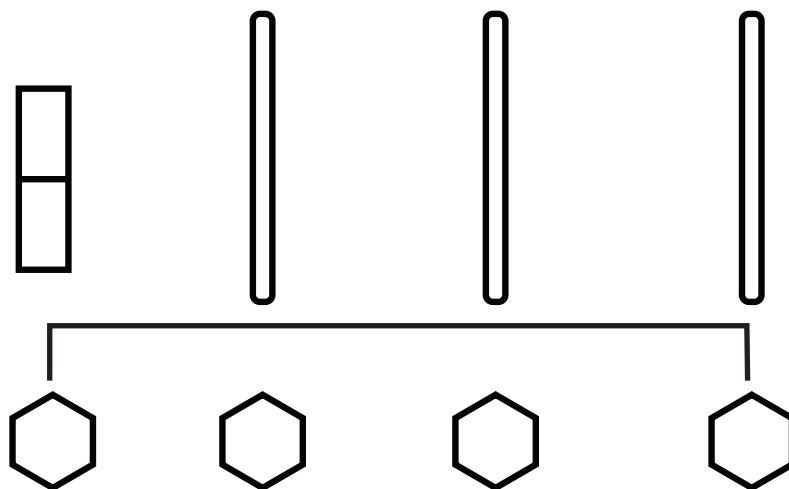

KBD


S/H

ADSR

VCO 2



VCO-2

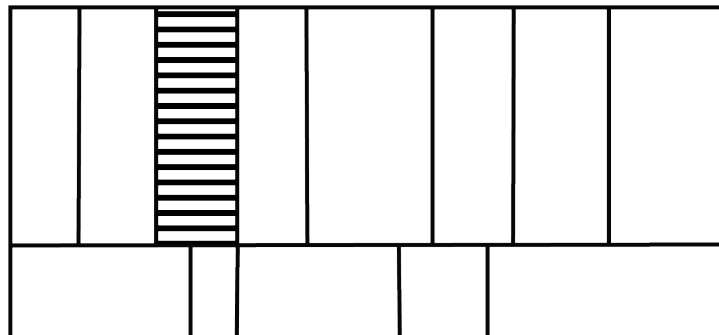

Frequency



Frequency

Fine Tune



Fine Tune

Pulse Width



Pulse Width

VCO-2

VCO-2

TRI

TRI



ST



ST

SINE

SINE




PLS




PLS

LFO

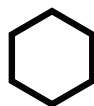


KBD

KBD

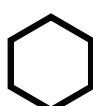

S/H


S/H

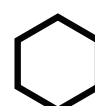

ADSR




ADSR

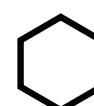

VCO1




VCO1

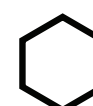

Noise

Noise

⋮ ⋮ ⋮ ⋮ ⋮ VCO-3

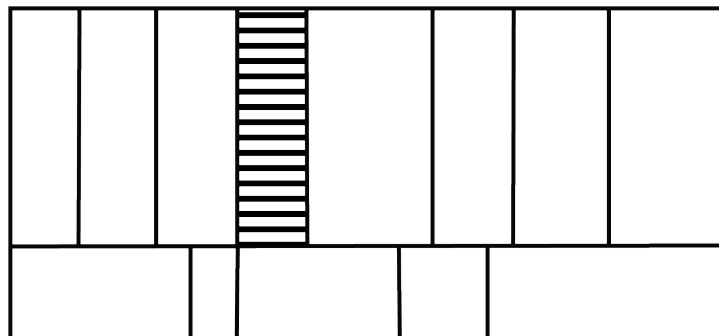

⋮ ⋮ ⋮ ⋮ ⋮ ⋮ ⋮

Frequency

⋮ ⋮ ⋮ ⋮ ⋮ ⋮ ⋮

Fine Tune

⋮ ⋮ ⋮ ⋮ ⋮ ⋮ ⋮

Pulse Width

VCO-3 ⋮ ⋮ ⋮ ⋮ ⋮

ST ⋮ ⋮ ⋮



PLS ⋮ ⋮ ⋮




⋮ ⋮ ⋮ LFO




⋮ ⋮ ⋮

KBD

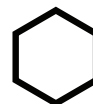


⋮ ⋮ ⋮

S/H

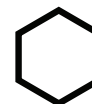

⋮ ⋮ ⋮



ADSR

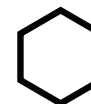


⋮ ⋮ ⋮

VCO2



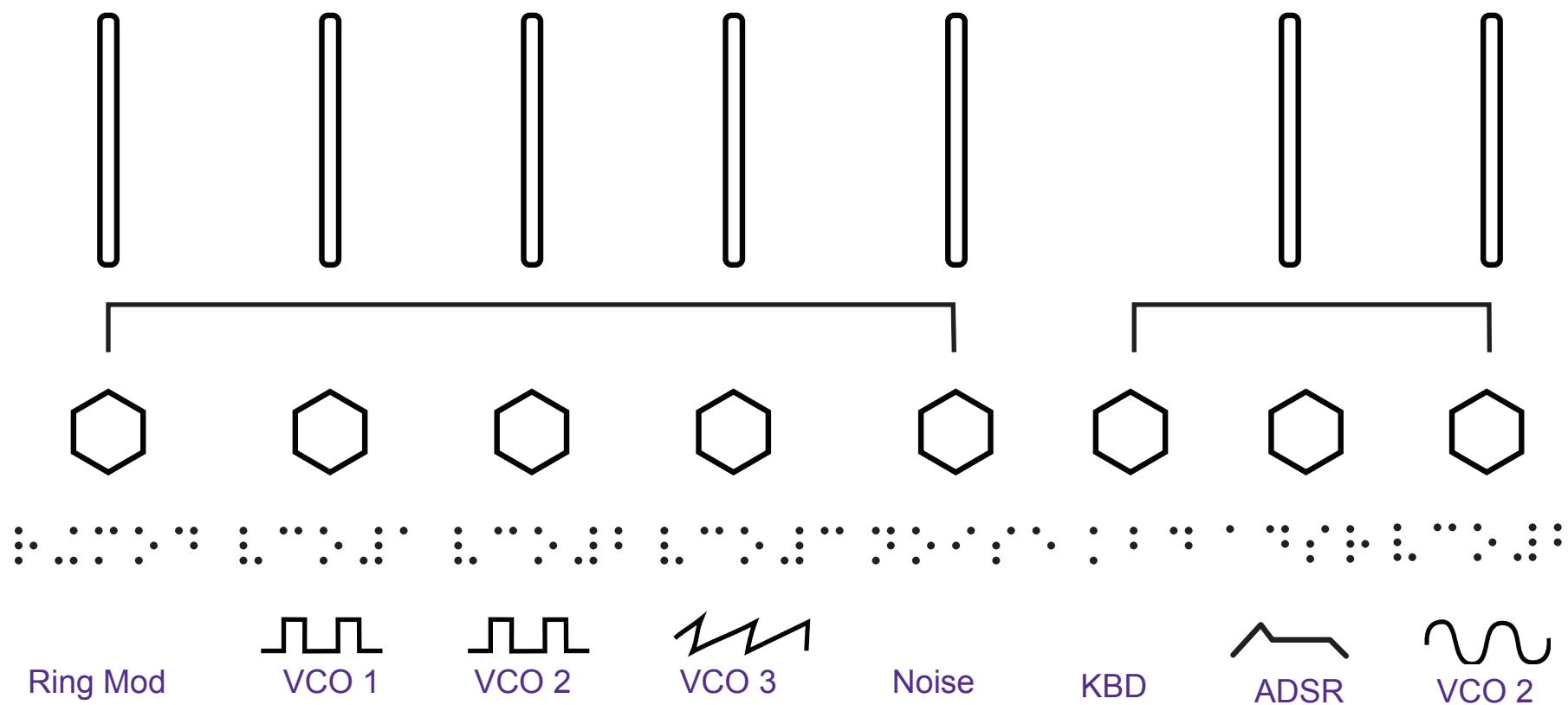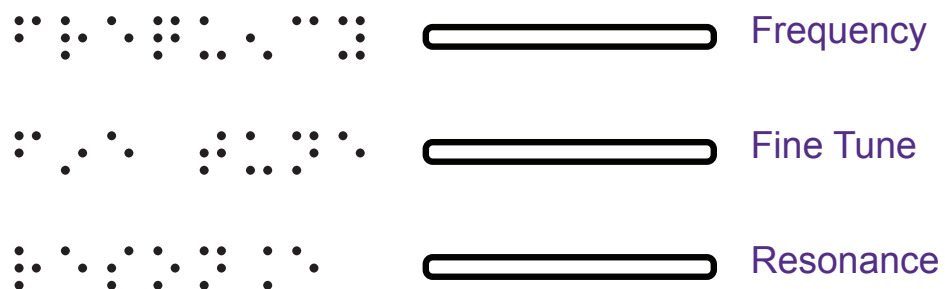

• •• •• ••• ADSR/AR

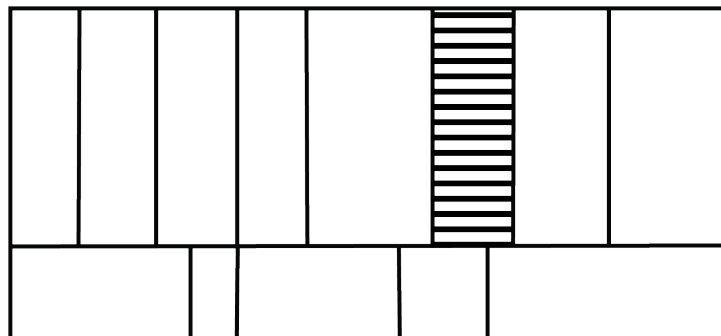

A



•

D



••

S



•••

R



••••

ADSR/AR

• •• •• •••



Attack

• •• •• •••

Start




Release

••• •• •••


KBD Gate /Trig

• •• •• ••• •••

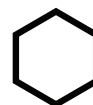


S/H Gate

• •• •• •••

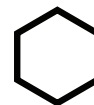


Gate

••• •••


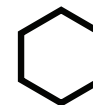


Trig

••• •••

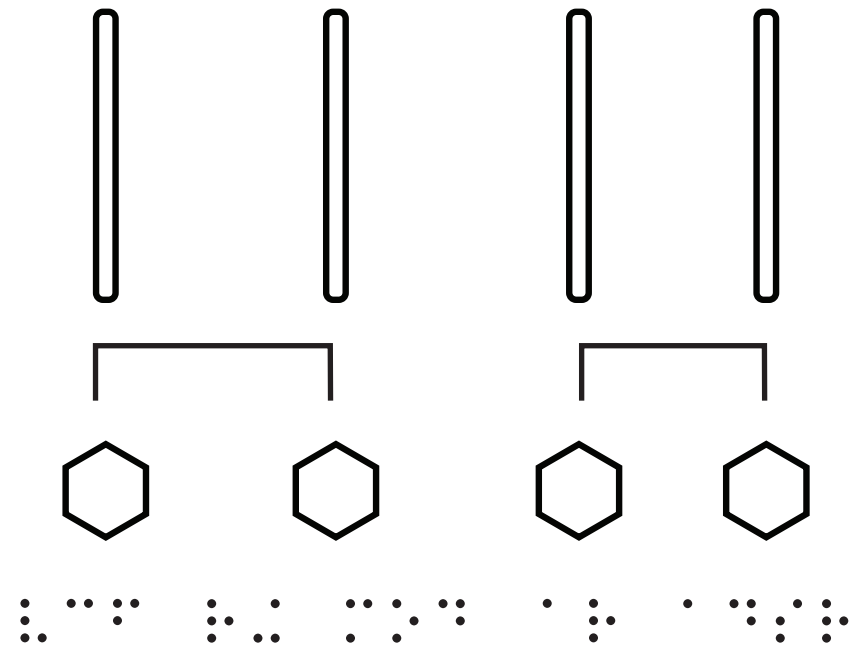




Mixer / Reverberator

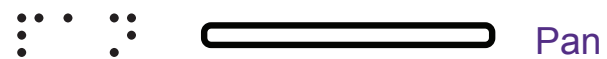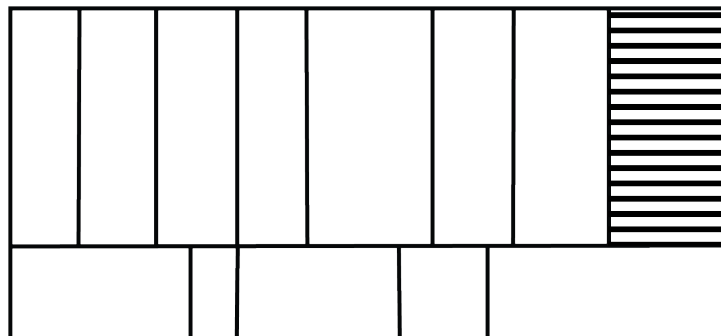

Mixer




Reverberator

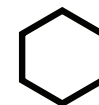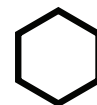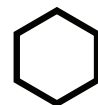

Reverb



VCF




VCA



Mixer

⋮ ⋮ ⋮ ⋮ ⋮ ⋮ ⋮ ⋮

Left Speaker


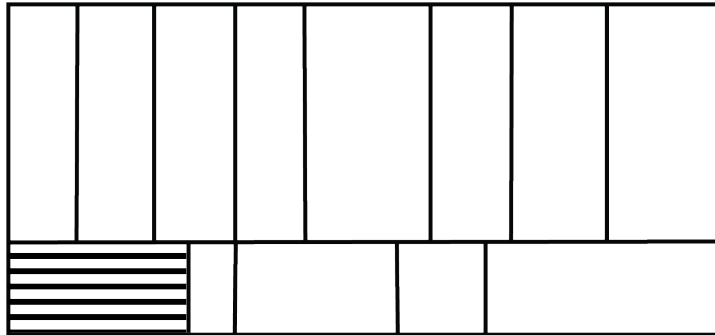


KBD ⋮ ⋮ ⋮




⋮ ⋮ ⋮ ⋮ ⋮ ⋮ ⋮ ⋮

Multiples

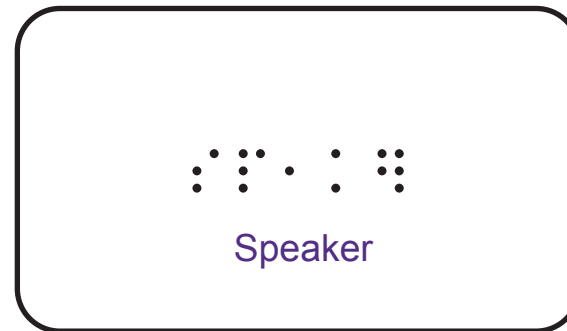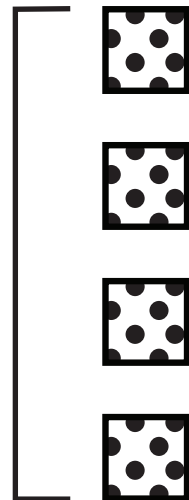


⋮ ⋮ ⋮ ⋮
⋮ ⋮ ⋮ ⋮
Left Speaker


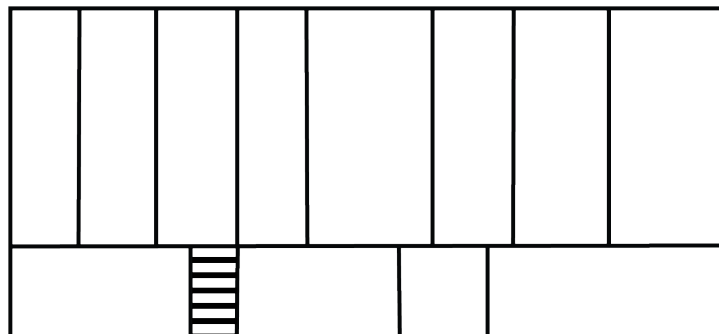



Noise Generator

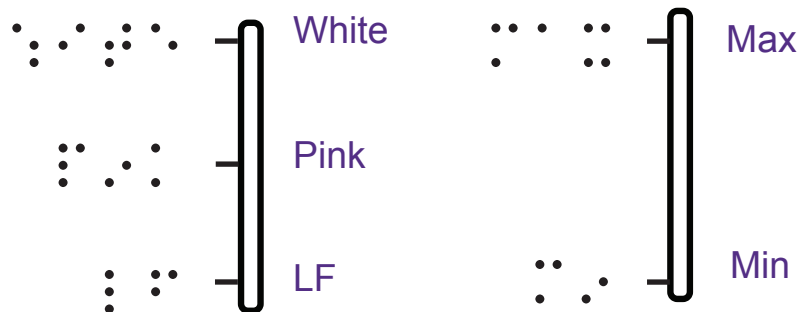The image shows three dot patterns. The first pattern consists of 10 dots arranged to form the number '1'. The second pattern consists of 10 dots arranged to form the number '2'. The third pattern consists of 10 dots arranged to form the number '3'.



Voltage Processors

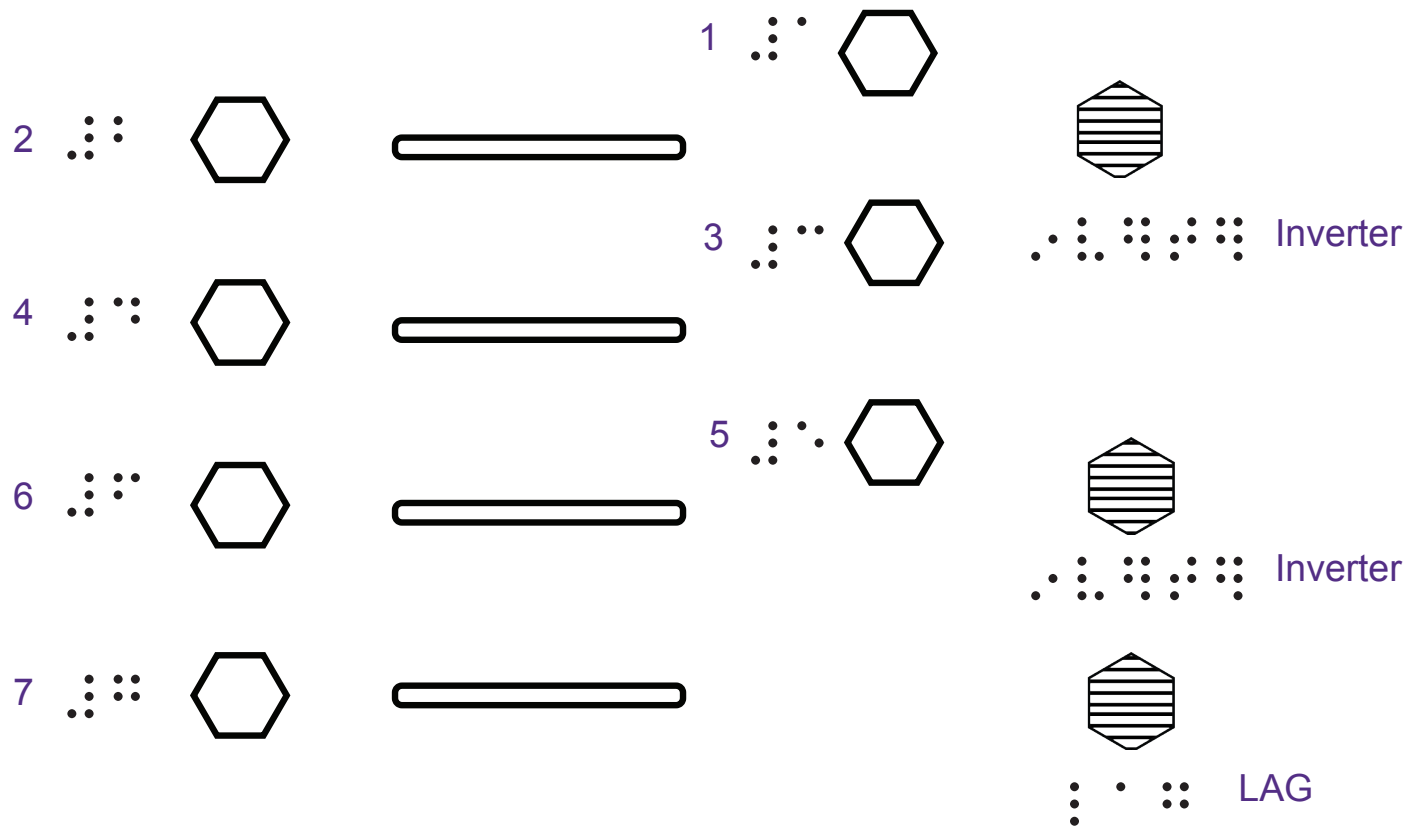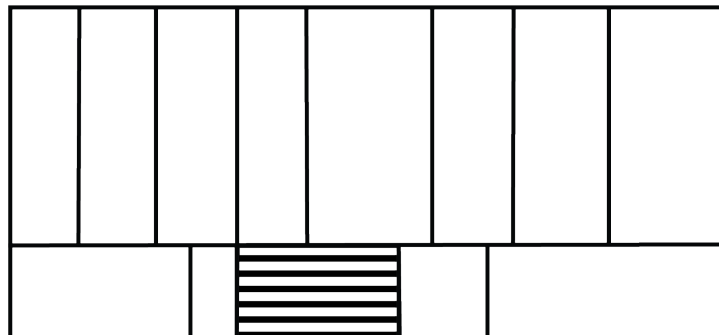


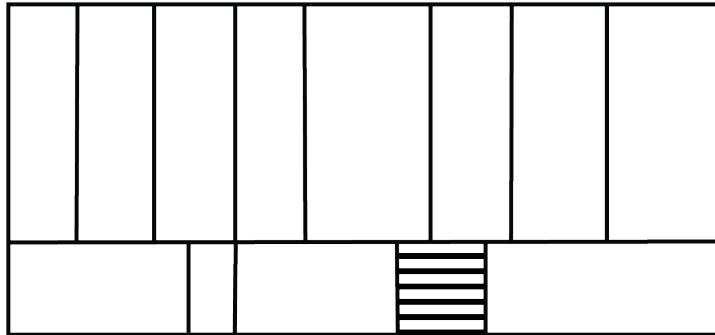

Sample and Hold

A 3x10 grid of dots forming a 3x10 rectangular array.

Noise

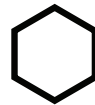

Int Clock




S/H

The image shows four groups of black dots arranged to represent the numbers 1, 2, 3, and 4. The first group has 1 dot, the second has 2 dots, the third has 3 dots, and the fourth has 4 dots.



Ext Clock

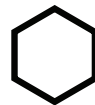

Level


Rate

Electronic Switch






Right Speaker

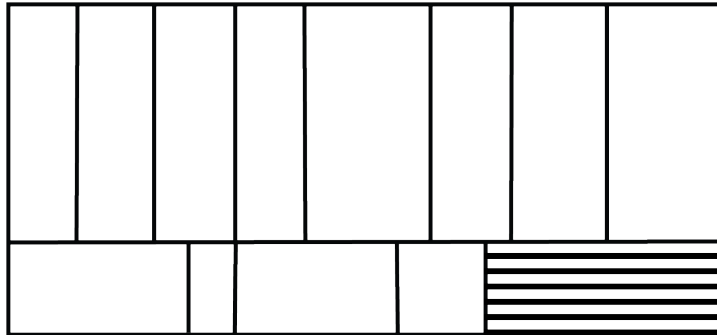

Right Speaker

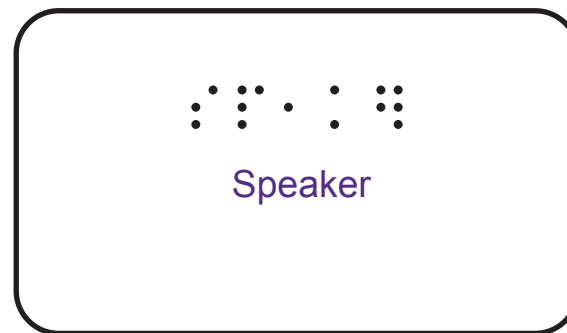

Power



Stereo Phones