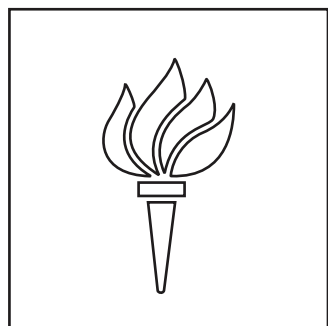


NYU Ability Project


Serge Modular 73-75 Panels



NYU


Ability
Project

NYU Ability Project

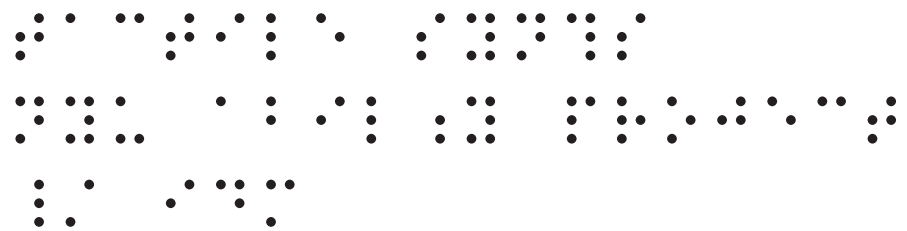

Tactile Synths

NYU Ability Project / IDM

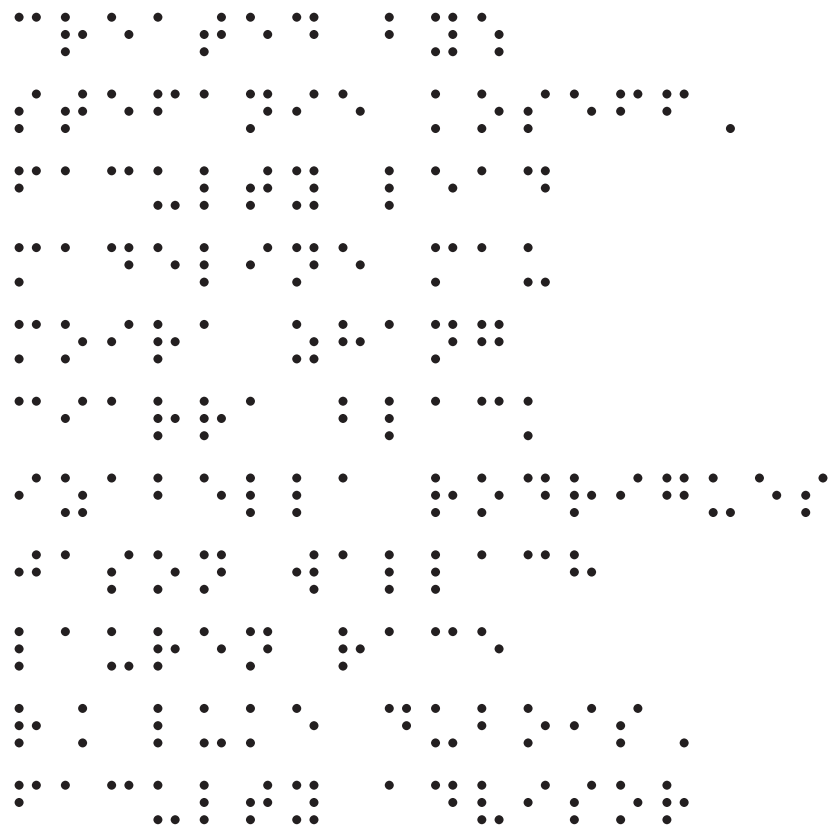

Created by:

Stefanie Koseff, Faculty Lead

Madeline Mau

Moirra Zhang

Ciarra Black

Izabella Rodrigues

Jason Wallach

Lauren Race

R. Luke DuBois, Faculty Advisor

panel guide

VOICE

VOICE

CONTROL

CONTROL

HOMEBUILT #1

HOMEBUILT #1

HOMEBUILT #2

HOMEBUILT #2

PRESET

PRESET

OSC

OSC

NOI

NOI

OSC

OSC

POS

POS

SEQ

SEQ

OSC

OSC

POS

POS

TWS

TWS

NEG

NEG

PRG

PRG

TWS

TWS

NEG

NEG

P&T

P&T

ENV

ENV

TBS

TBS

VCF

VCF

COM

COM

COM

COM

ENV

ENV

ENV

ENV

VCA

VCA

PRC

PRC

PRC

PRC

ENV

ENV

ENV

ENV

VCA

VCA

SSG

SSG

VCA

VCA

ADP

ADP

ADP

ADP

RING

RING

RING

RING

RING

RING

RING

RING

RING

RING

ENV

ENV

ENV

ENV

ENV

ENV

ENV

ENV

ENV

ENV

ADP

ADP

ADP

ADP

PRE

PRE

PRE








PRE

PRE

PRE



table of contents

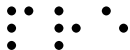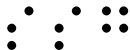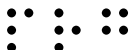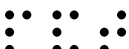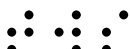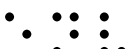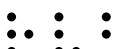 KEY	 1	 NOI	 5	 PRE	 10	 SSG	 16
 ADP	 2	 OSC	 6	 PRG	 11	 TBS	 17
 COM	 2	 P&T	 7	 RING	 14	 TWS	 18
 ENV	 3	 POS	 8	 RVB	 14	 VCA	 19
 NEG	 4	 PRC	 9	 SEQ	 15	 VCF	 19

KEY


symbol key



ac in



misc in

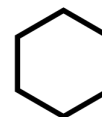

trs in



ac out



misc out



trs out



dc in



basic knob



dc out



offset (+) knob



pulse in



scale (x) knob



pulse out



button

ADP

adapter



a out



a in



b out



b in



c out



c in

COM

triple comparator

Braille header for the COM section



a in 1



a thresh



b in 1



b thresh



c in 1



c thresh




a out



a in 2




b out

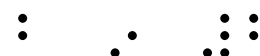

b in 2



c out

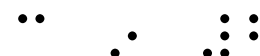


c in 2

ENV

envelope generator



end

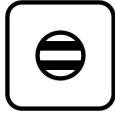

out



window



start in



out



window +



cycle



hold



window vc



duration vc



rise



fall



duration x

⠠⠠⠠⠠⠠ NEG

⠠⠠⠠⠠⠠⠠⠠⠠⠠⠠ negative slew



⠠⠠⠠⠠⠠ a vc



⠠⠠⠠⠠⠠ a in



⠠⠠⠠⠠⠠ a out



⠠⠠⠠⠠⠠ a x



⠠⠠⠠⠠⠠ a end



⠠⠠⠠⠠⠠ a out



⠠⠠⠠⠠⠠ a +



⠠⠠⠠⠠⠠ a end



⠠⠠⠠⠠⠠ b vc



⠠⠠⠠⠠⠠ b in



⠠⠠⠠⠠⠠ b out



⠠⠠⠠⠠⠠ b x



⠠⠠⠠⠠⠠ b end



⠠⠠⠠⠠⠠ b out



⠠⠠⠠⠠⠠ b +



⠠⠠⠠⠠⠠ b end

NOI

noise source



white



white



pink



pink



s/h ac



s/h dc



stepped ac



stepped dc



manual



trigger

OSC

oscillator



sine ac



ws x



sine dc



waveshape



saw dc



saw ac



fm



fm



fm x



fm x



sync



frequency

⠠⠠⠠⠠⠠ P&T

⠠⠠⠠ ⠠⠠⠠ ⠠⠠⠠⠠⠠⠠ peak & trough



⠠⠠⠠ ⠠⠠⠠

peak out



⠠⠠⠠⠠⠠⠠ ⠠⠠⠠

trough out



⠠⠠⠠ ⠠⠠⠠

peak out



⠠⠠⠠⠠⠠⠠ ⠠⠠⠠

trough out



⠠⠠⠠ ⠠⠠⠠ ⠠⠠⠠

peak in



⠠⠠⠠⠠⠠⠠ ⠠⠠⠠ ⠠⠠⠠

trough in



⠠⠠⠠ ⠠⠠⠠ ⠠⠠⠠

peak in



⠠⠠⠠⠠⠠⠠ ⠠⠠⠠ ⠠⠠⠠

trough in



⠠⠠⠠ ⠠⠠⠠ ⠠⠠⠠

peak in



⠠⠠⠠⠠⠠⠠ ⠠⠠⠠ ⠠⠠⠠

trough in



⠠⠠⠠ ⠠⠠⠠ ⠠⠠⠠

peak in



⠠⠠⠠⠠⠠⠠ ⠠⠠⠠ ⠠⠠⠠

trough in

POS

positive slew



a vc



a in



a out



a x



a start



a high



a +



a sustain



a end



b vc



b in



b out



b x



b start



b high



b +




b sustain



b end


PRC

dual processor

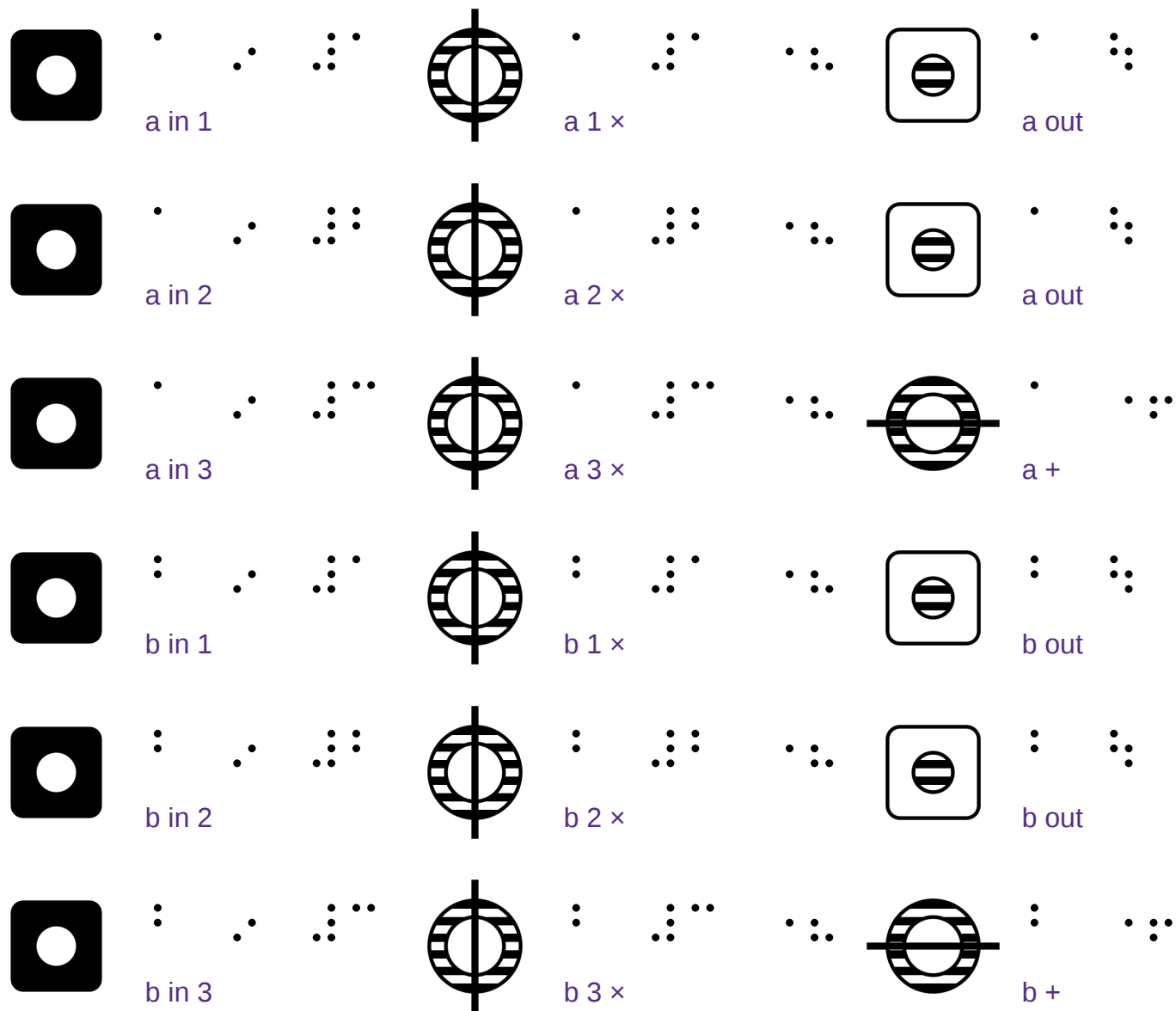

PRE

preamplifier

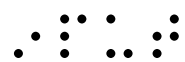

input




gain



out



out

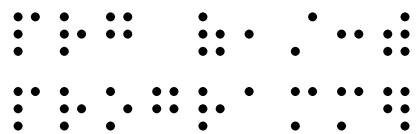

PRG (1/3) programmer



1 out



2 out



3 out



4 out



1 a



2 a



3 a



4 a



1 b



2 b



3 b



4 b



1 c



2 c



3 c



4 c



1 in




2 in




3 in



4 in

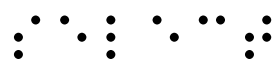


select

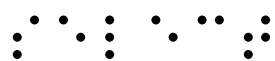


select



select

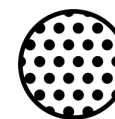

select

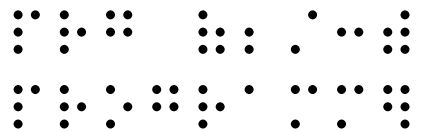

PRG (2/3) programmer



5 out



6 out



7 out



8 out



5 a



6 a



7 a



8 a



5 b



6 b



7 b



8 b



5 c



6 c



7 c



8 c



5 in



6 in




7 in



8 in




select

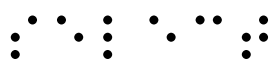

select



select

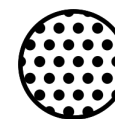

select

PRG (3/3)
programmer



all out




all out



cv a out




cv a out

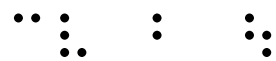

cv b out



cv b out


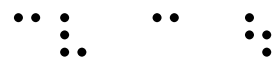


cv c out



cv c out

RING

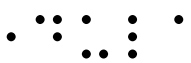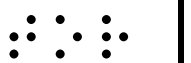ring modulator





out





y



vc y





x



vc x



x - xy

RVB

reverberator





out





out



mix



wet



wet






in

SEQ

sequencer

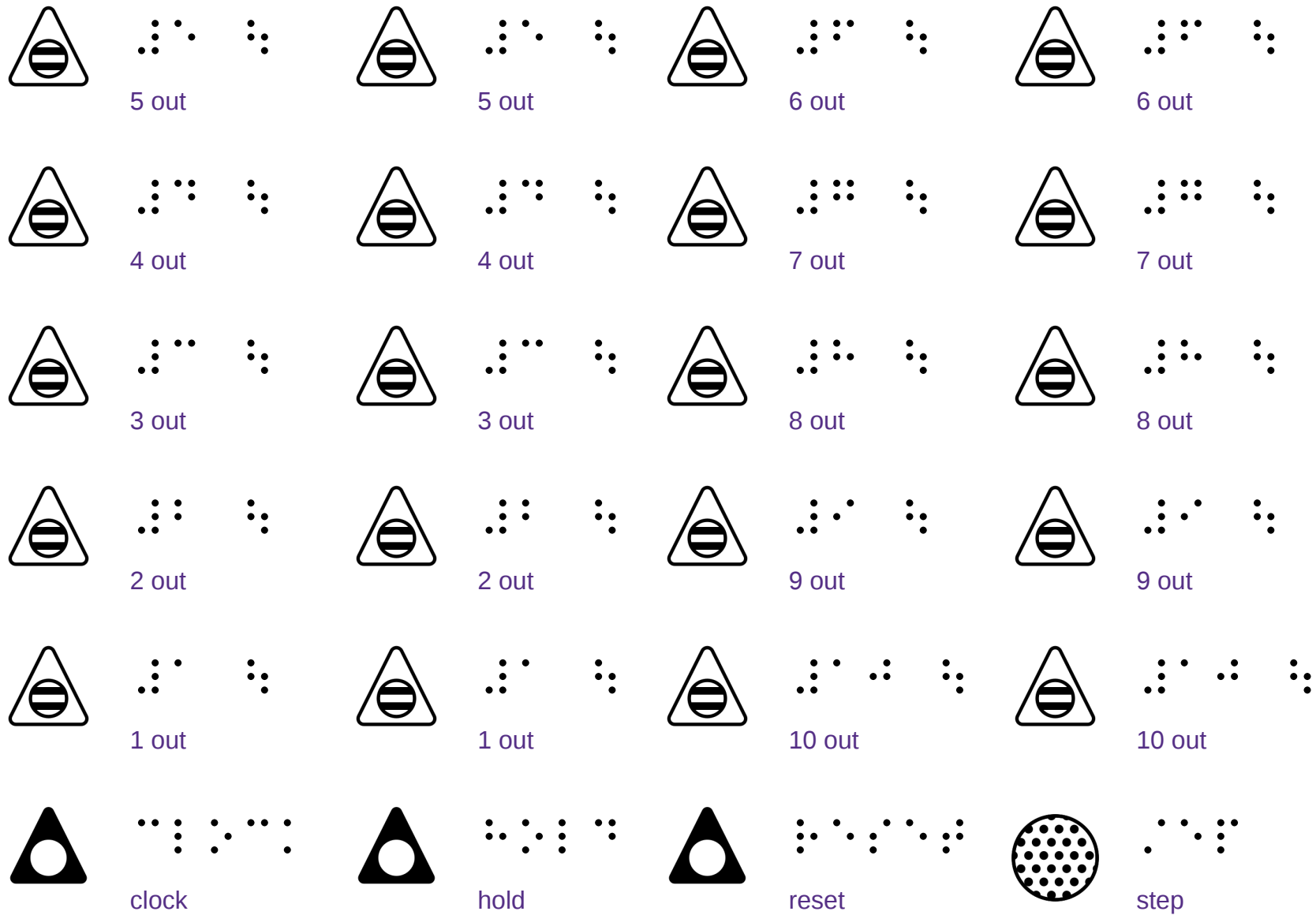

SSG

smooth & stepped generator

smooth & stepped generator



smooth vc



smooth out



smooth x



cycle



smooth in



smooth +



hold



coupler



stepped vc



sample



coupler



stepped x



cycle



stepped in



stepped +



stepped out



bi-directional router



TWS

triple waveshaper



a vc1



a vc2



a out




a x



a in




a out

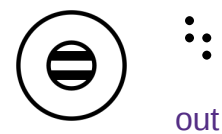


out



ac

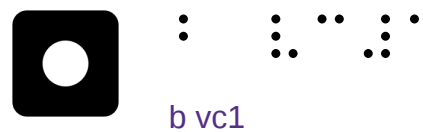

b vc1

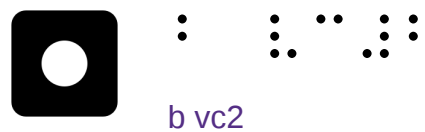


b vc2



b out



dc

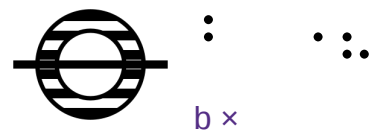

b x




b in



b out



lin

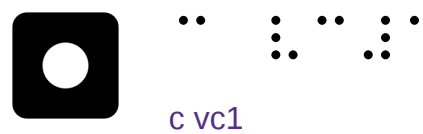

c vc1




c vc2



c out




log

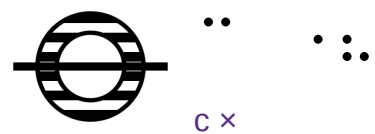

c x



c in

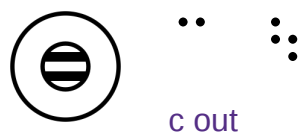

c out



gain

VCA gate

VCF filter



high



high



band



band




low




low




Q

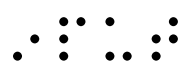

input

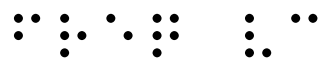


freq vc

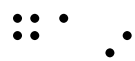

gain



freq x

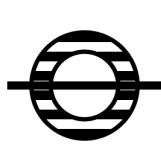

frequency